

Lab 5. Research on DC drive PWM converters

Student name: _____Zhu Chenhao_____

Date of submission__08/04/2025__

HDU ID _____22320630_____

Student ITMO ID__375462_____

Part 1. Evaluate missing parameters

- Open Actuators_Lab_5_R2022b.slx model and Actuators_Lab5_R20XX.mlx

- Source data

$U_{s_rated} =$	65	- Rated source voltage, V;
$n_{rated} =$	600	- Rated rotating speed, rpm;
$f_{sw} =$	3500	- PWM frequency, Hz;
$R_a =$	0.005	- Resistance of DC machine winding, Ω ;
$L_a =$	0.554e-3	- Armature inductance, H;
$J_s =$	0.238	- Moment of inertia, $kg \cdot m^2$;
$I_{a_rated} =$	50	- Anchor rated current of DC machine, A;
$k_{i_lim} =$	2.2	- Maximum current limit, A.

Evaluations:

$P = U_{s_rated} \cdot I_{a_rated} =$	3250	- Power, W;
$I_{a_sc} = \frac{U_{s_rated}}{R_a} =$	764.7059	- Short circuit current, A;
$\omega_{m_rated} = \frac{2 \cdot \pi \cdot n_{rated}}{60} =$	62.8319	- Rated rotating speed, rad/s;
$k_e = \frac{(U_{s_rated} - R_a \cdot I_{a_rated})}{\omega_{m_rated}} =$	0.9669	- EMF constant, V*s/rad;
$k_m = k_e$		- Electromechanical constant, N · m /A;
$T_{e_rated} = k_m \cdot I_{a_rated} =$	48.3443	- Rated Torque of the DC machine, N · m;
$T_{e_max} = k_{lim} \cdot T_{e_rated} =$	106.3553	- Maximum torque, N · m;
$T_{e_st} = k_m \cdot I_{a_sc} =$	739.3683	- Starting torque, N · m;
$K_{eff_rated} = \frac{\omega_{m_rated} \cdot T_{e_rated}}{P} \cdot 100\% =$	93.4615	- Rated efficiency, %;
$\tau_e = \frac{L_a}{R_a} =$	0.0065	- Electromagnetic time constant, s;
$\omega_0 = \frac{U_{s_rated}}{k_e} =$	67.2275	- Idle speed, rad/s;
$\tau_m = \frac{J_s \cdot \omega_0}{T_{e_st}} =$	0.0216	- Electromechanical time constant, s

Part 2. Evaluate parameters of the system with PWM

Transistor switched on circuit parameters

$V_{fvt} = 0$	- IGBT Forward voltage V_f at current $I_a \approx 0$, [V] (For MOSFET may be considered equal to 0);
$V_{fvtIa} = 2.2$	- Forward voltage V_f at current $I_a = I_{lim} = I_{a_rated} \cdot k_{lim}$, [V];
$R_{onvt} = \frac{(V_{fvtIa} - V_{fvt})}{I_{lim}} = 0.02$	- MOSFET / IGBT resistance R_{on} , [Ω];

Snubber circuit parameters

$C_S = 330e-9$	- Snubber capacitance, [F];
$R_S = 1e6$	- Snubber resistance, [Ω];

Reverse (antiparallel) diode parameters

$V_{f_{rd}} = 0.85$	- Internal (antiparallel) diode forward voltage V_f at current $I_a \approx 0$, [V];
$V_{f_{rdIa}} = 0.95$	- Internal (antiparallel) diode forward voltage at current I_{lim} , [V];
$R_{on_{rd}} = \frac{(V_{f_{rdIa}} - V_{f_{rd}})}{I_{lim}} = 9.09e4$	- Internal (antiparallel) diode resistance R_d , [Ω];


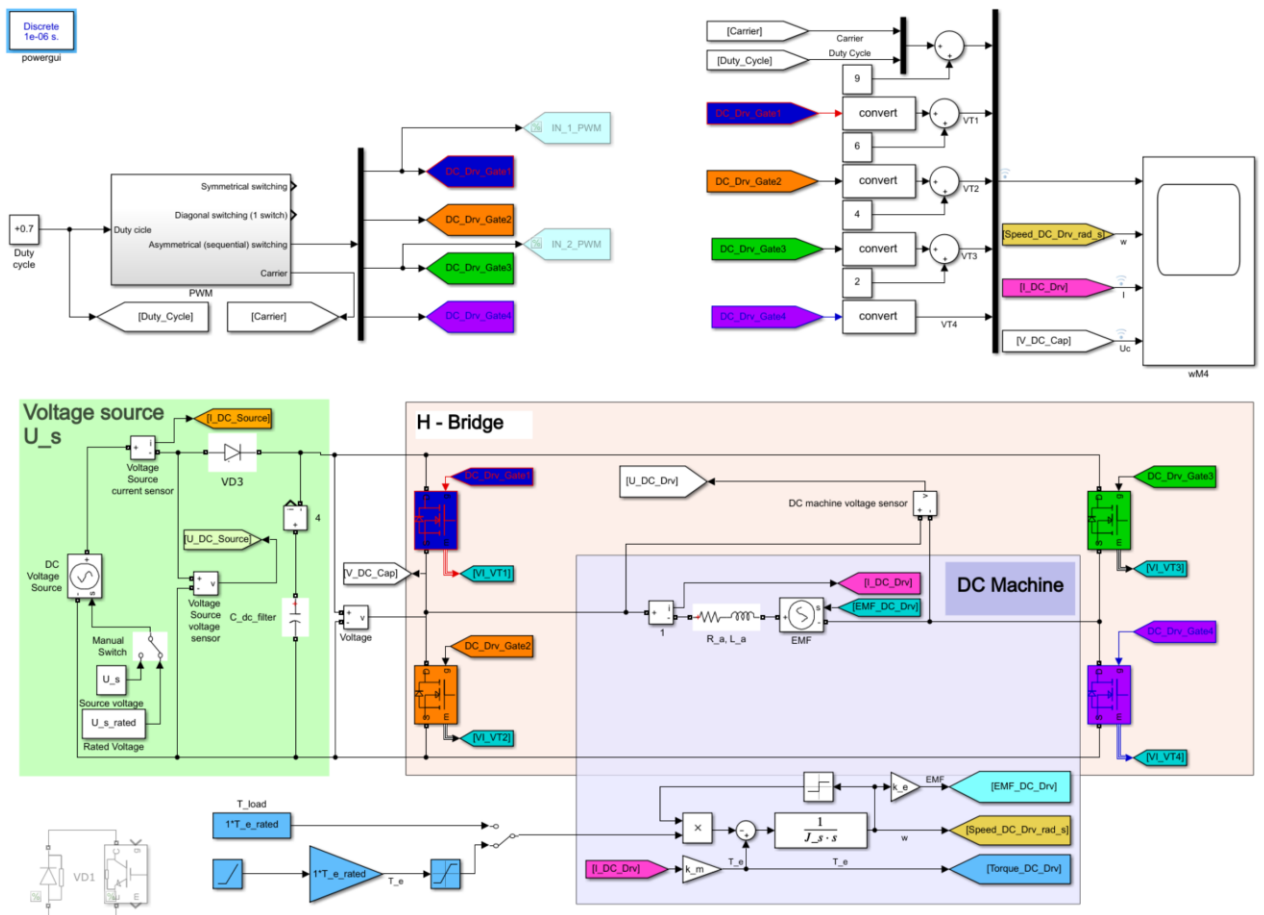



Figure 1 – DC drive system under test

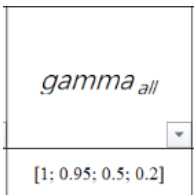
Part 3. Simulation results

NB! Duty cycles values are in your variant data: as γ_{all} values.



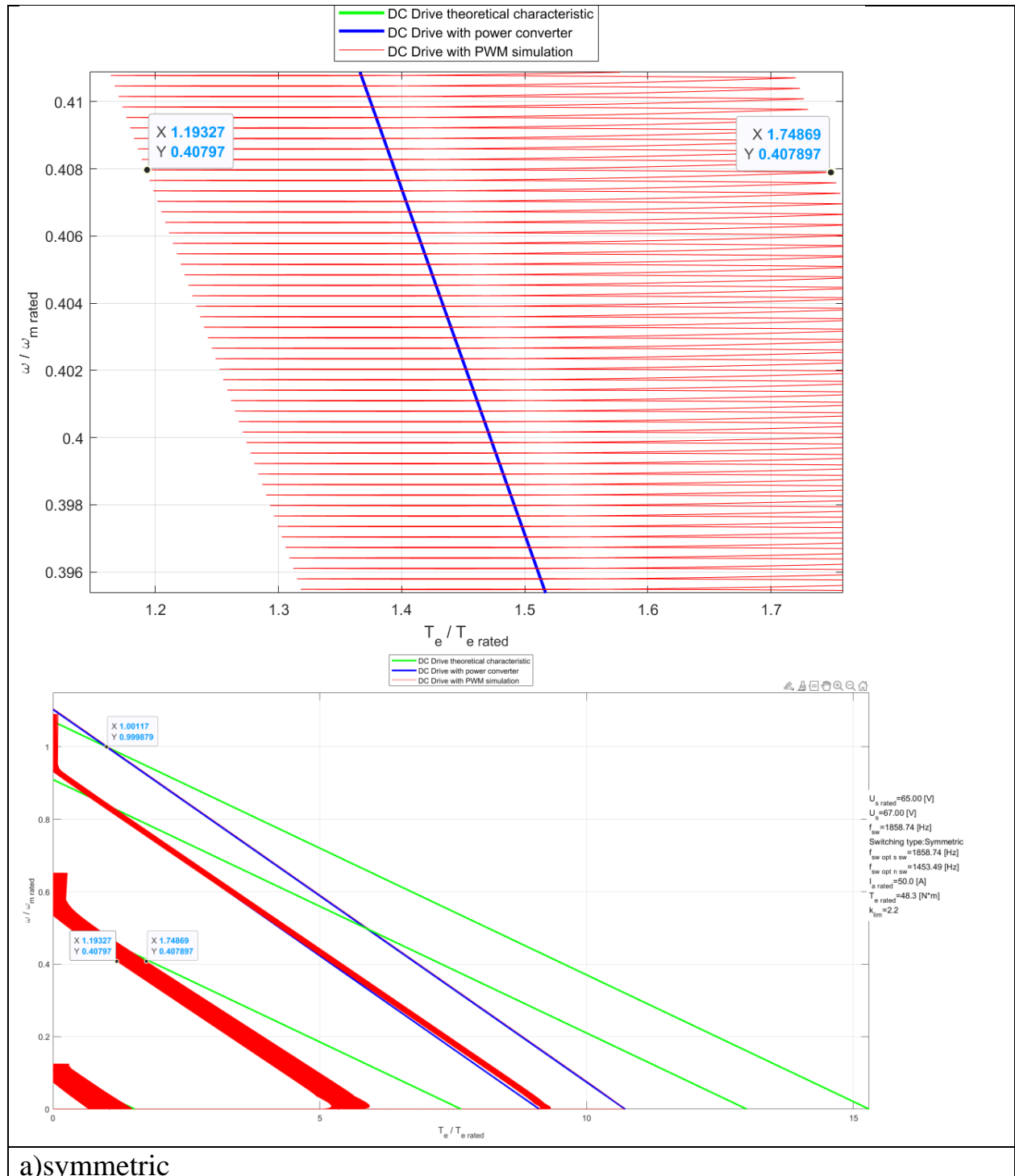- Compare diagonal (one switch) and symmetric switching



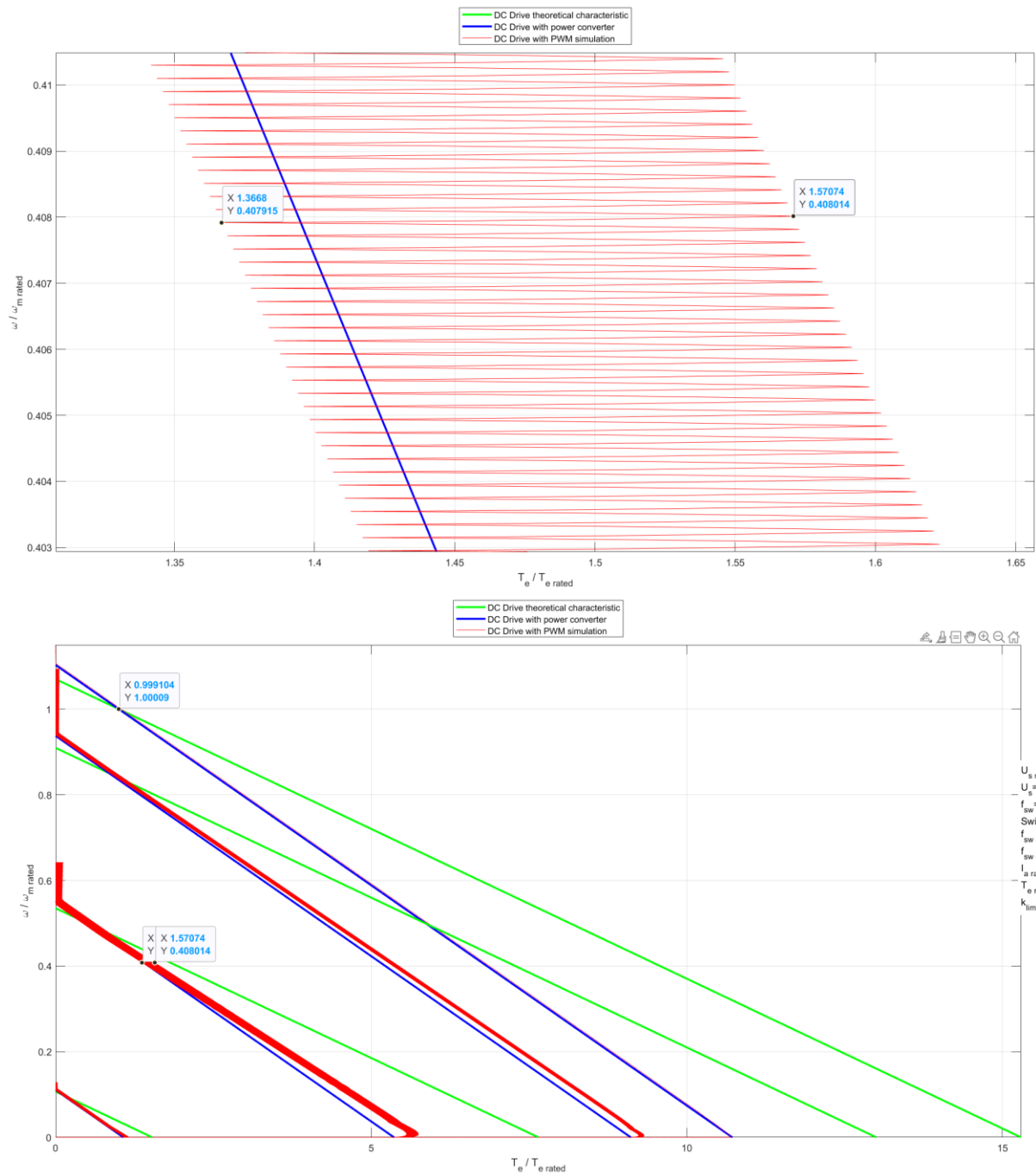

b) asymmetric sequential

Part 4. Simulation results

- Analyze drive parameters with different pulse width with duty cycle $\gamma = 0.75$ and $T_{load} = k_{lim} * T_{e_rated}$

Symmetric	Diagonal	Asymmetric sequential
PWM diagram	PWM diagram	PWM diagram
DC Voltage U_s [V]	DC Voltage U_s [V]	DC Voltage U_s [V]
DC machine current I_a [A]	DC machine current I_a [A]	DC machine current I_a [A]
DC machine speed ω [rad/s]	DC machine speed ω [rad/s]	DC machine speed ω [rad/s]
Converter efficiency	Converter efficiency	Converter efficiency
DC drive efficiency	DC drive efficiency	DC drive efficiency

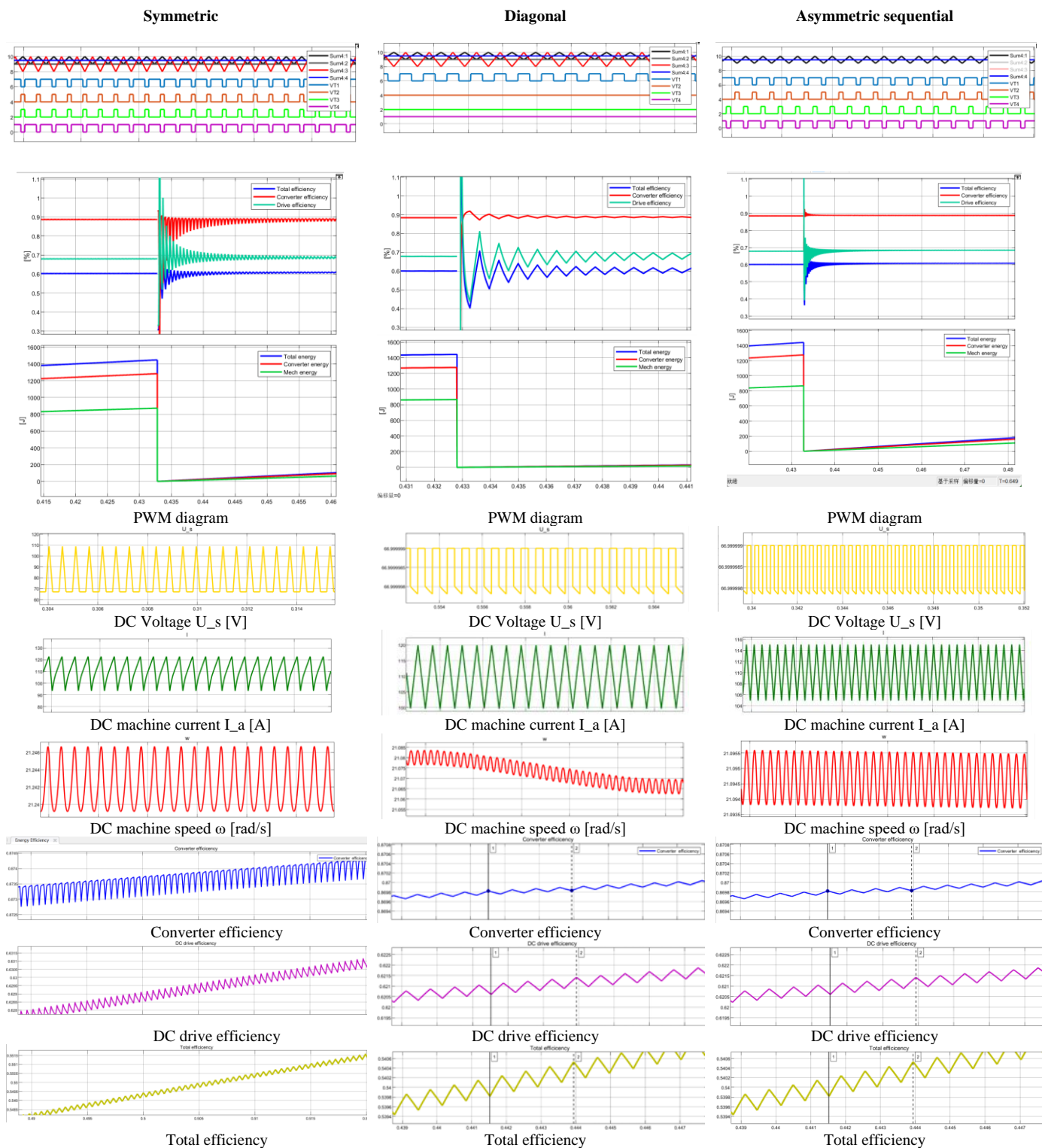
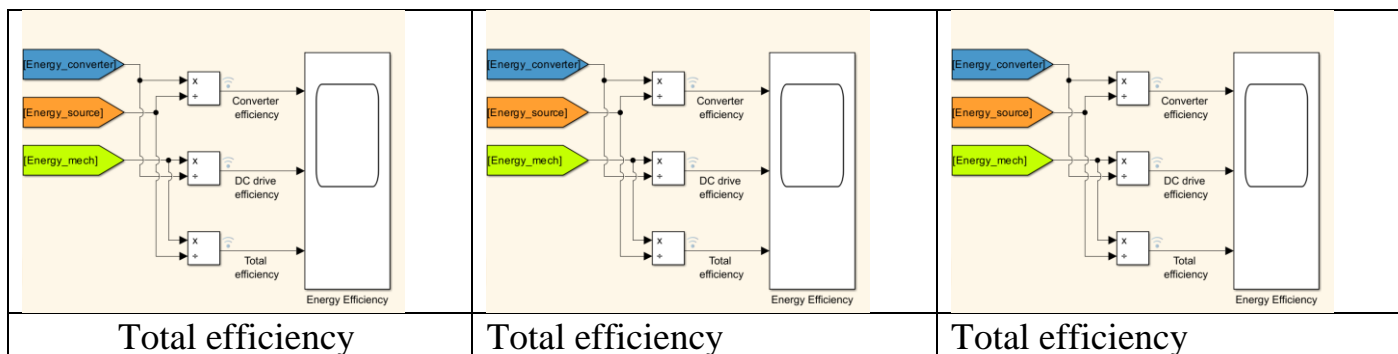


Figure 3 – DC Drive with PWM converter efficiency

Optimal switching frequency evaluation (symmetrical switching)

$$f_{sw_opt} = 0.332 \sqrt[3]{\frac{\alpha_K r_a^2}{L_a^2(t_+ + t_-)}} = 1858.736 \text{ Hz}$$

Optimal switching frequency evaluation (non-symmetrical sequential and diagonal switching)

$$f_{sw_opt} = 0.26 \sqrt[3]{\frac{\alpha_K r_a^2}{L_a^2(t_+ + t_-)}} = 1453.488 \text{ Hz}$$

- **Analyze drive parameters with different pulse width with**
- **duty cycle (gamma)= 0.75 and $T_{load}=T_{e_max} = k_{lim} * T_{e_rated}$**

Conclusions

Results of comparison efficiency, current and speed ripple in case of symmetrical, diagonal, and sequential switching.

Performance at $\gamma = 0.75$, $T_{load}=T_{e_max}$

- Symmetric switching:
 - Lowest voltage (U_s) and current (I_a) ripple.
 - Peak efficiency near optimal switching frequency (1858.7 Hz).
- Diagonal switching:
 - Significant current ripple due to asymmetric current paths.
 - Efficiency drops by 5–8% (higher switching and conduction losses).
- Asymmetric sequential switching:
 - Intermediate performance, suitable for specific load conditions.

Optimal Switching Frequency Analysis

- Symmetric switching allows a higher optimal frequency (1858.7 Hz) due to uniform loss distribution.
- Asymmetric strategies require lower frequencies (1453.5 Hz) to minimize losses caused by unbalanced current paths.

Symmetric switching:

- Advantages: High efficiency, low ripple, stable speed.
- Best for: Precision control (e.g., servo systems).

Diagonal switching:

- Advantages: Simpler circuitry.
- Drawbacks: Low efficiency, high ripple (suitable only for cost-sensitive applications).

Asymmetric sequential switching:

- Trade-off: Balances efficiency and complexity (ideal for dynamic loads).